

R F Z E - O S > X U

$$K_1 = \frac{11110101100}{S \quad 1 \quad X} \quad 6$$


$$K_2 = \frac{0011010111100}{F \quad I \quad V \quad E} \quad 5$$

So the differential equation is

$$\frac{d^2 y}{dt^2} - 6 \frac{dy}{dt} + 5y = 0$$

Circuit (Using differentiator circuits of op-amps)

→ I have made the circuit

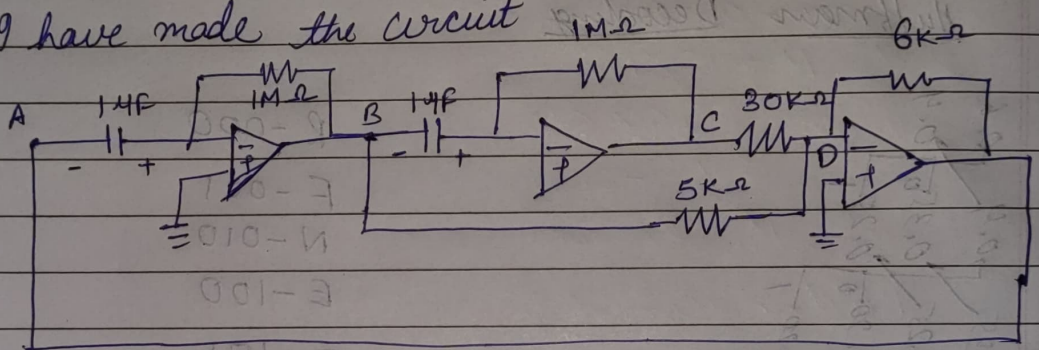

→ Let at A $V_{in} = y$

$$\text{So at B } V_B = -10^{-6} \times 10^6 \frac{dy}{dt} = -\frac{dy}{dt}$$

$$\text{At B } V_B = -\frac{dy}{dt}$$

$$\begin{aligned} \text{So at C } V_C &= -10^{-6} \times 10^6 \frac{dV_B}{dt} \\ &= \frac{d^2 y}{dt^2} \end{aligned}$$

Now at B, C, D we have an adder circuit

$$-6 \times 10^3 \left(\frac{1}{30 \times 10^3} \frac{d^2 y}{dt^2} - \frac{1}{5 \times 10^3} \frac{dy}{dt} \right) = y$$

$$\boxed{\frac{d^2 y}{dt^2} - 6 \frac{dy}{dt} + 5y = 0} \rightarrow \text{Required diff eq}^n.$$

→ Now for initial conditions

let v_c be voltage across at $t=0$ across 1st capacitor so $V_A + v_c = 0$ (According to polarity)
 $y|_{t=0} + v_c = 0.$

$$\boxed{v_c = -2V}$$

let v_b be voltage at $t=0$ across 2nd capacitor
 so $-\frac{dv_b}{dt} + \frac{dv_c}{dt} = 0$

$$\boxed{\frac{dv_b}{dt} = 5V}$$

⇒ From the graph $y(t) = 6$ at $t \approx 1ns$